

Ex 1: 7pts

$I_{AB} = ?$ by using Thevenin Theorem.

1) $E_{Th} = ?$ & $R_{Th} = ?$

$E_{Th} = R \cdot I$ (1) (0,5pts)

$I = \frac{E}{R_1 + R_3 + R_4}$ (2) (0,5pts)

eq(2) in eq(1), we obtain:

$E_{Th} = \frac{R_4}{R_1 + R_3 + R_4} \cdot E$ (1pt)

NA: $E_{Th} = \frac{10}{5+5+10} \cdot 30 = 15V$ (0,5pt)

$R_{Th} = ?$

$R_{Th} = [(R_1 + R_3) \parallel R_4] + R_2 + R_5$ (1pt)




NA: $R_{Th} = [(5+5) \parallel 10] + 4 + 6 = 15\Omega$ (0,5pt)

$I_{AB} = ?$

$I_{AB} = \frac{E_{Th}}{R_{Th} + R_L}$ (1pt)

NA: $I_{AB} = \frac{15}{15+5} = \frac{15}{20} = 0,75A$


$I_{AB} = 0,75A$ (1pt)

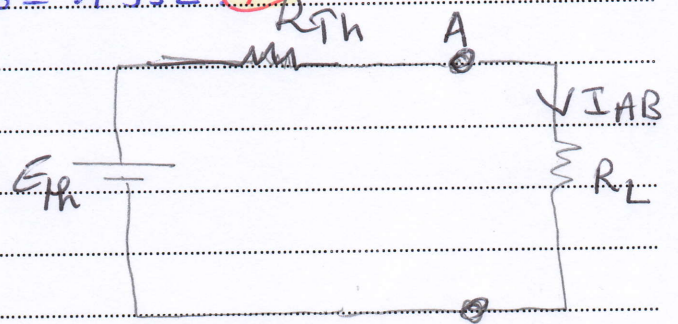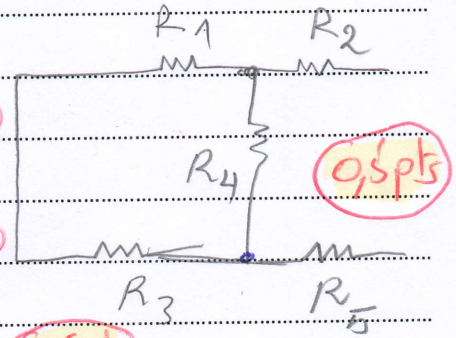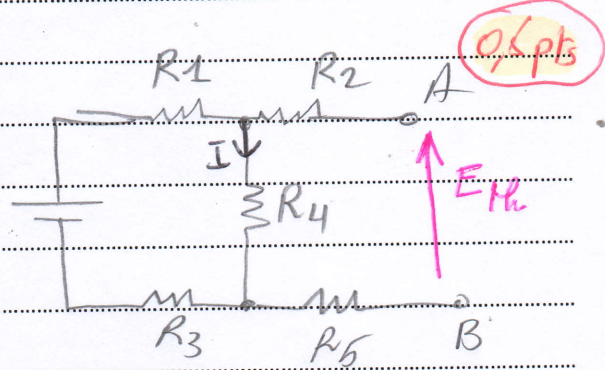

Ex 2: (7 pts)

$I_4 = ?$ by using superposition theorem.

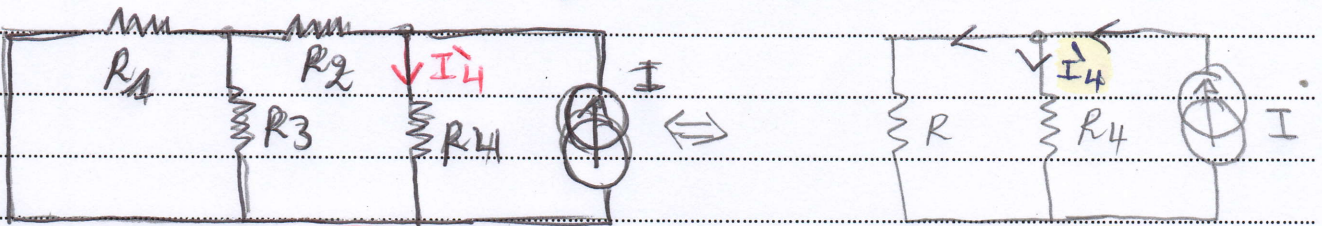1) 1st case: The voltage source E is discarded. $I_4' = ?$ (2,25)



0,5 pts


0,25 pts

$$R = R_2 + (R_1 \parallel R_3) = 10 + \frac{5 \times 10}{5 + 10} = 13,33 \Omega \quad (0,5 \text{ pts})$$

by using current divider: $I_4' = \frac{R}{R + R_4} \cdot I$ (0,5 pt)

NA: $I_4' = \frac{13,33}{13,33 + 20} \cdot 4 = 1,6 \text{ A}$

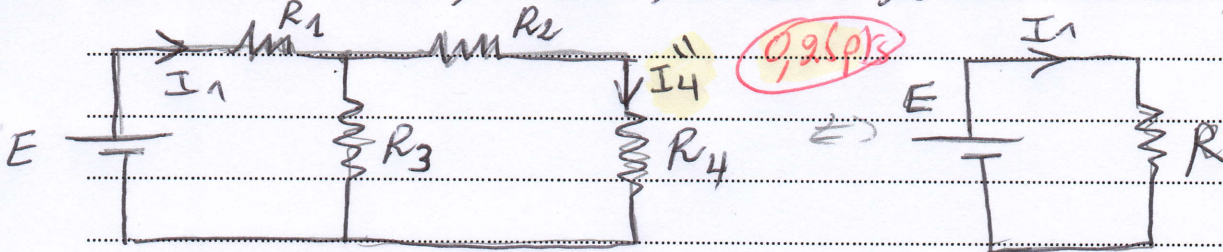2) 2nd case: The current source I is discarded. $I_4'' = ?$ (4,75)



0,25 pts

by using current divider $I_4 = \frac{R_3}{R_3 + (R_2 + R_4)} I_1$ (0,5 pts)

$$R = [(R_2 + R_4) \parallel R_3] + R_1 \quad (1) \quad (0,5 \text{ pts})$$

NA: $E = R I_1 \Rightarrow I_1 = E / R \quad (2) \quad (0,5 \text{ pts})$

eq (2) in eq (1): $I_1 = E / [(R_2 + R_4) \parallel R_3] \quad (3) \quad (0,5 \text{ pts})$

eq (3) in eq (1), we obtain:

$$I_4'' = \frac{R_3}{R_3 + (R_2 + R_4)} \cdot \frac{E}{(R_2 + R_4) \parallel R_3} \quad (0,5 \text{ pts})$$

NA: $R = 30 \parallel 10 + 5 = 12,5 \Omega \quad (0,5 \text{ pts})$

$$I_4'' = \frac{10}{10 + 10 + 20} \cdot \frac{20}{12,5} = 0,4 \text{ A} \quad (0,5 \text{ pts})$$


$$I_4 = I_4' + I_4'' \quad (0,5 \text{ pts})$$

NA: $I_4 = 1,6 + 0,4 = 2 \text{ A}$

$I_4 = 2 \text{ A}$

0,5 pts

Ex 3 (6 pts)

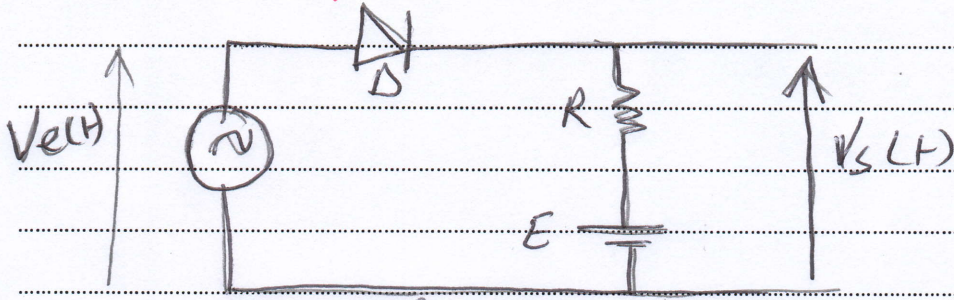

Circuit Analysis

- 1] A^+
 $\rightarrow v_e(t) > 5V \Rightarrow D \text{ on} \Rightarrow v_s(t) = v_e(t)$ (1.5 pts)
 $\rightarrow v_e(t) < 5V \Rightarrow D \text{ off} \Rightarrow v_s(t) = 5V$ (1.5 pts)

- 2] $A^- \Rightarrow D \text{ off} \Rightarrow v_s(t) = 5V$ (1.5 pts)

