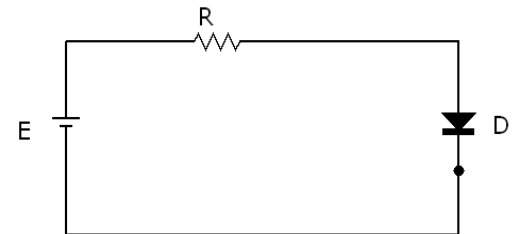


## Recitation 1 : PN Junction Diode

### Exercise 1

For the following circuit, calculate R value.


**Given:**  $V_0=0.62V$ ,  $E=2V$ , and  $I=100mA$ .


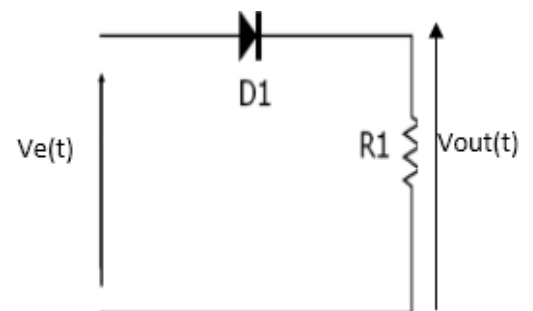
### Exercise 2


For the following circuit, draw the voltage Vs for  $v_m = 10V$  ;  
 1V and 0.3V.

**Given:**  $R=1000 \Omega$ ;  $V_0=0.7V$ ;  $v(t) = v_m \sin \omega t$



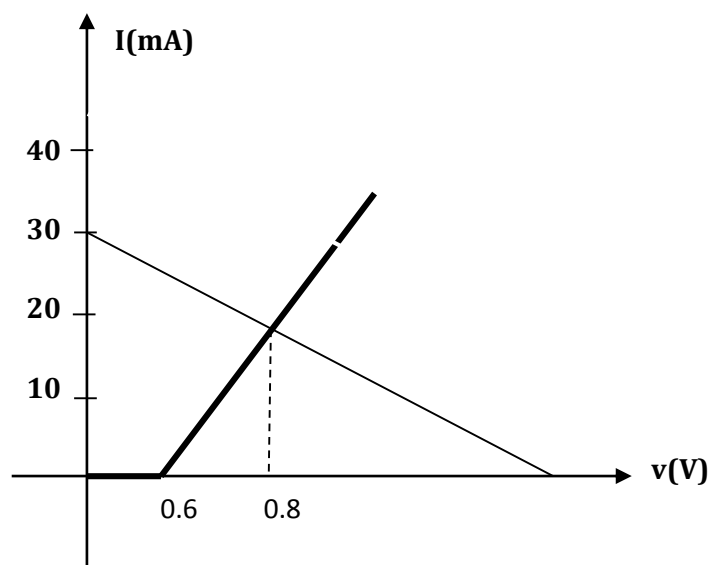
### Exercise 3

Let D a PN junction diode, its characteristic can be approximated by the figure below.



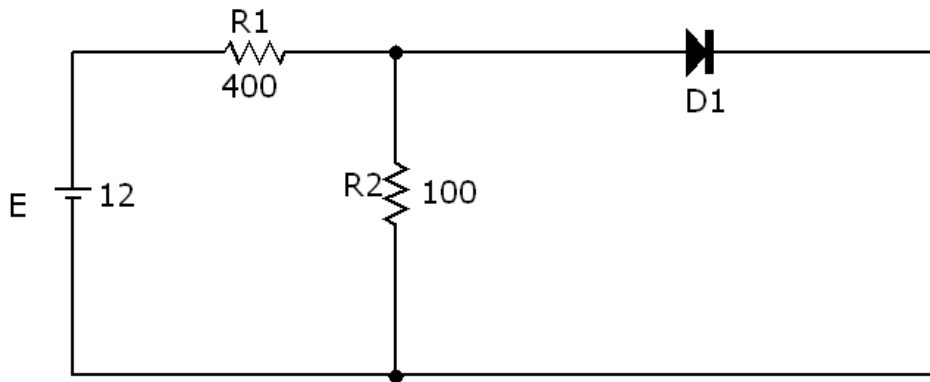
The diode "D" is used in the circuit given in the figure below.



1. Write the diode load line equation.
2. Determine the operating point graphically Q.

**Exercise 4**

In the following circuit, the diode is perfect (ideal), draw the graphs  $V_e(t)$  and  $V_S(t)$ . Given  $V_e(t)=12\sin\omega t$

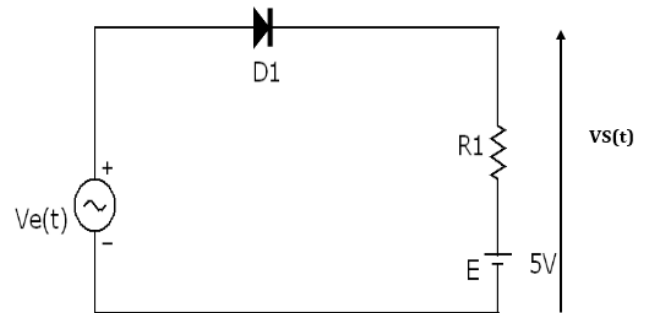

**Exercise 5**

Consider the circuit in the figure below. Trace the shape of the signal  $V_S$  when  $V_e(t)$  has the form shown in figure 2:

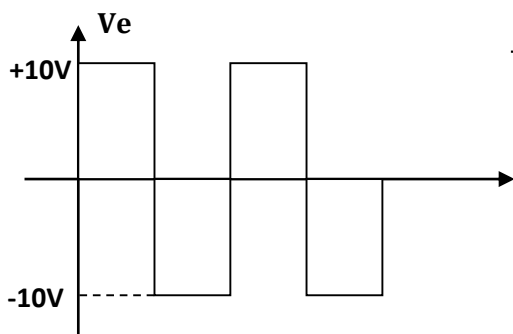


Figure 1

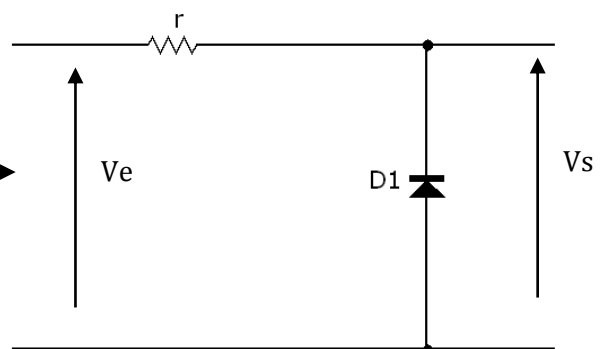



Figure 2

**Exercise 6**

---

We consider circuit given in the Figure below in which diode D has a zero threshold voltage and a negligible dynamic resistance.

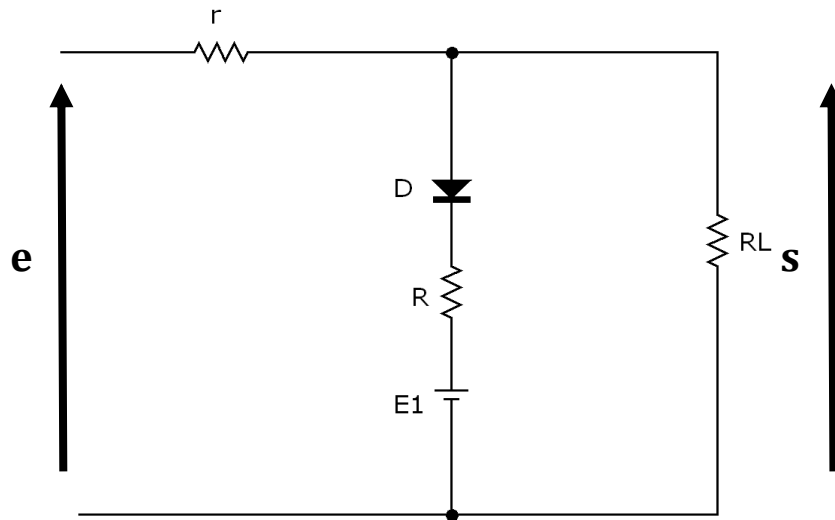**Given:**  $r=100\Omega$ ,  $R_L=1K\Omega$ ,  $R=250\Omega$ ,  $E_1=3V$ .



1. We consider the diode D is blocked

1.1. Give the equivalent diagram of the circuit

1.2. Determine a relationship between  $r$ ,  $e$ ,  $s$  and  $R_L$  then give the numerical expression of  $s$  as a function of  $e$ .

2. We consider the diode D is passed

2.1. Give the equivalent diagram of the circuit

2.2. Determine a relationship between  $r$ ,  $e$ ,  $s$ ,  $E_1$ ,  $R_L$  and  $R$  of  $s$  as a function of  $e$ .