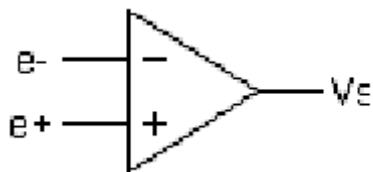


Recitation 5 : Operational Amplifier (AO)

In all the circuits considered in these exercises, the operational amplifier is assumed to be ideal: infinite input resistance (zero input current) and infinite open loop differential amplification (zero differential voltage).




$e+$: voltage of the + input (non-inverting input) of the operational amplifier.

$e-$: input voltage - (inverting input) of the operational amplifier.

Exercice 1


We consider the circuit below :

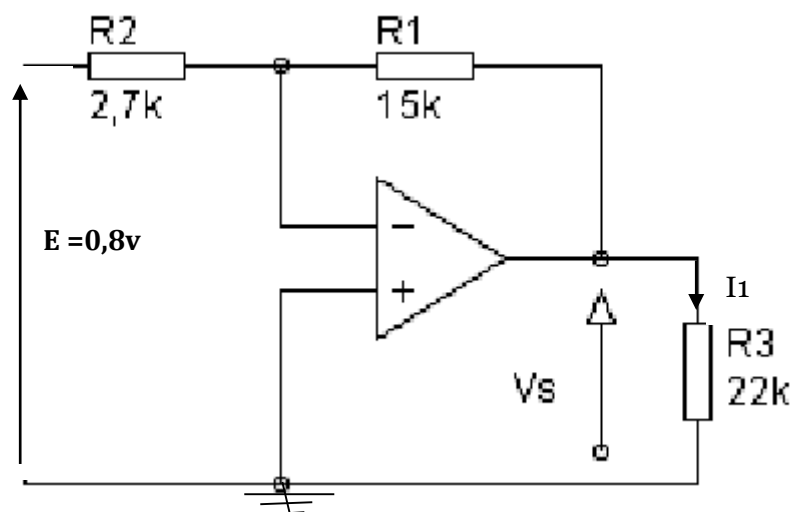

- Calculate the current flowing in R3.

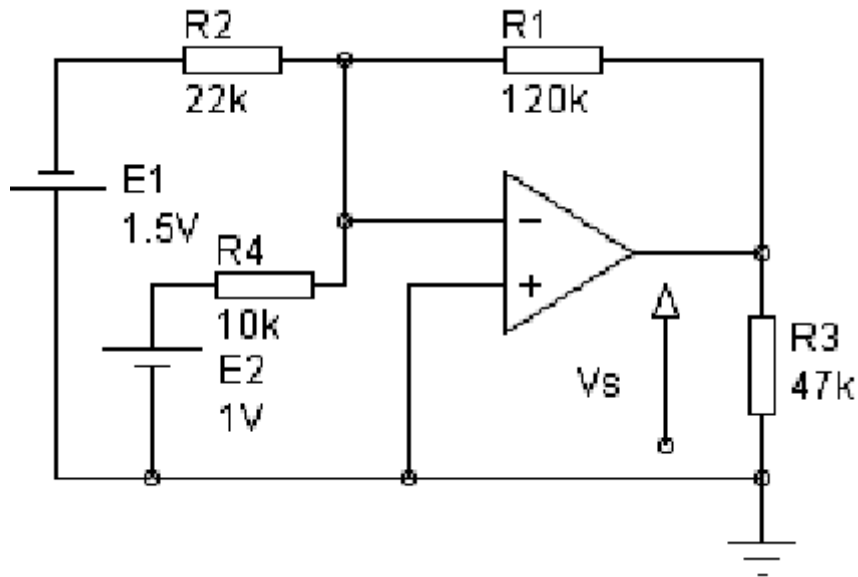Exercise 2

We consider the circuit based on OA given by the figure below:



- Calculate the voltage V_s according to: E_1 , E_2 and the circuit resistances.

Exercise 3

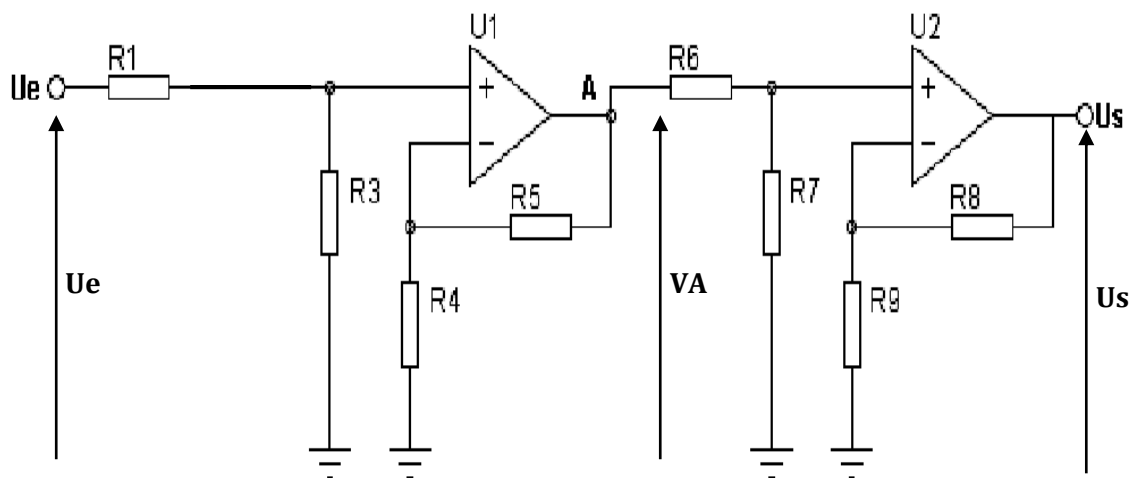


Figure 1

1. Give the expressions for U_A/U_e , U_s/U_A as a function of the resistances.
2. Calculate the circuit gain: U_s/U_e .

Exercice 4

Consider the circuit in the figure below:

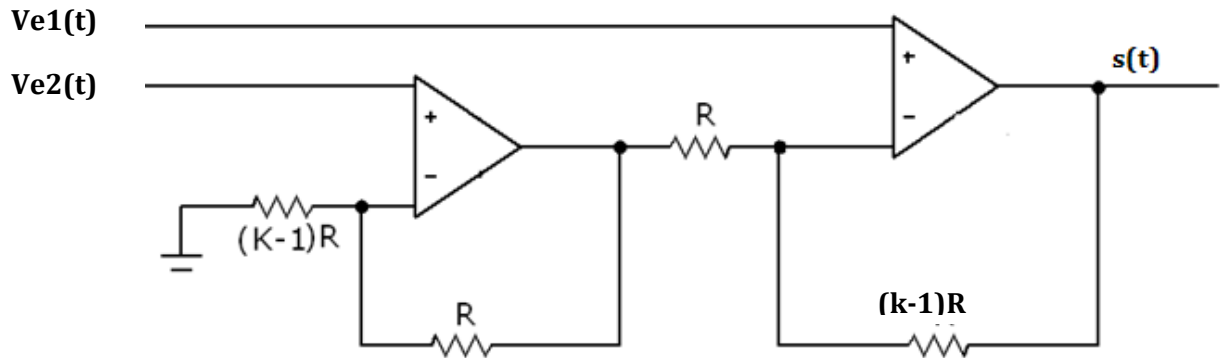


Figure 2

1. Give the relationship which links the output voltage $s(t)$ to the input voltages $V_{e1}(t)$ and $V_{e2}(t)$.
2. How should we choose the constant K to have $s(t)=10\sin\omega t$ for $V_{e1}(t)=2\sin\omega t$ and $V_{e2}(t)=\sin\omega t$?