

Chapter II
Conductors in electrostatic equilibrium

Course 4

II.6.4 Energy Stored in a Capacitor

Electric energy of a capacitor refers to the stored energy within a capacitor due to the accumulation of electric charge on its plates when it is connected to a voltage source. This energy is stored in the electric field between the capacitor's plates and can be released when the capacitor is connected to a circuit. The energy stored in a capacitor is given by the formula:

$$W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{1}{2}\frac{Q^2}{C}$$

In this case, $V = \Delta V$ it refers to the potential difference (also known as voltage) between the two plates of the capacitor.

II.6.5 Association of Capacitors

In practice, systems are found consisting of a set of capacitors connected in series or in parallel which can be substituted by a single capacitor and vice versa. The objective of grouping capacitors:

- To have a capacitor capable of withstanding high voltage differences.
- Or to have a capacitor with very large capacitance.

The characteristics of the equivalent capacitor can be determined as follows:

a- Series Combination

Let's consider N capacitors connected in series with capacitances $C_1, C_2, \dots, C_N$, respectively. These can be replaced by an equivalent capacitor with capacitance C_{eq} . In series combination, all capacitors carry the same charge Q.



The potential difference (voltage) between A and B is given by: $V_{AB} = V_1 + V_2 + V_3 + \dots + V_N$

All capacitors carry the same charge Q, which results in:


$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} + \dots + \frac{Q}{C_N} \Rightarrow \frac{Q}{C_{eq}} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N} \right)$$
$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

Then, the equivalent capacitance C_{eq} of a system composed of N capacitors in series, each

with capacitance C_i , is given by: $\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i}$

b- Parallel Combination

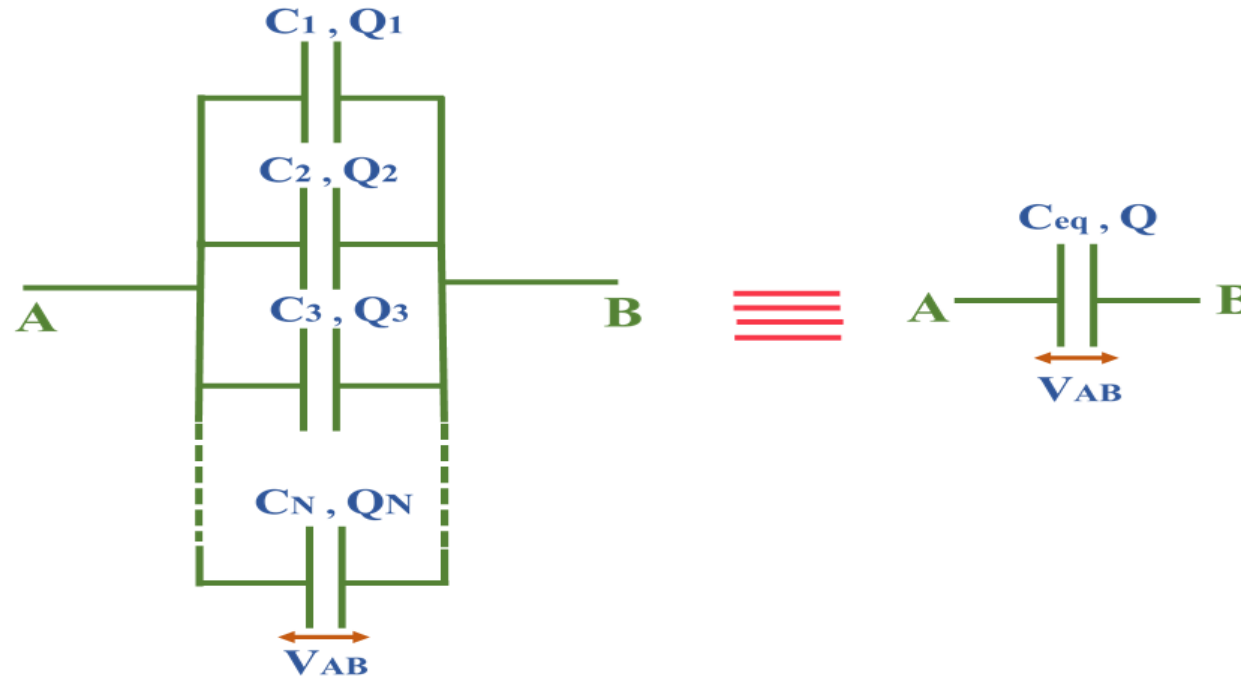When capacitors are connected in parallel, the voltage across each of them is equal.



In this case, the equivalent capacitor will have the charge Q .

$$Q = Q_1 + Q_2 + Q_3 + \dots + Q_N$$

$$C_{eq} V_{AB} = V_{AB} C_1 + V_{AB} C_2 + V_{AB} C_3 + \dots + V_{AB} C_N \Rightarrow C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

Then, the equivalent capacitance C_{eq} of a system composed of N capacitors in parallel, each


with capacitance C_i , is given by:

$$C_{eq} = \sum_{i=1}^N C_i$$

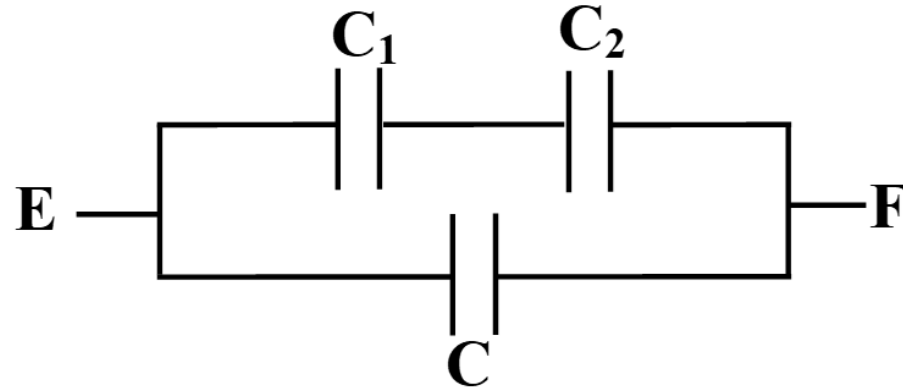Example:

Consider the arrangement of capacitors in the diagram below.

Given that $C_1 = 6 \mu\text{F}$, $C_2 = 3 \mu\text{F}$, and $C = 2 \mu\text{F}$.



- 1- Calculate the equivalent capacitor between E and F.
- 2- We apply a voltage between E and F of $V_{EF} = 1000$ volts. Find the charge carried by the equivalent capacitor, deduce the charge carried by capacitors C, C_1 , and C_2 .

Solution :

1- Calculate C_{eq} :

$$C_1 \text{ in series with } C_2: \frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} \rightarrow C' = 2 \mu\text{c}$$

$$C' \text{ in parallel with } C \rightarrow C_{eq} = C + C' = 4 \mu\text{c}$$

2- Find the charge carried by the equivalent capacitor, deduce the charge carried by capacitors C , C_1 , and C_2

✓ C_{eq} Deducted from C in parallel with $C' \Rightarrow (C_{eq}, C \text{ and } C' \text{ have same voltage})$

$$\Rightarrow Q = C V_{EF} = 2 \cdot 10^{-3} \text{ c}$$

✓ C_1 in series with $C_2 \Rightarrow (C', C_1 \text{ and } C_2 \text{ have same charge})$

$$\Rightarrow Q_1 = Q_2 = Q' = C' V_{EF} = 2 \cdot 10^{-3} \text{ c}$$