
Chapter 5: The Junction Field Effect Transistor

JFET

1. Introduction

A junction field effect transistor, TEC in French and is called JFET in English (Junction Field Effect Transistor). Unlike bipolar transistors whose operation is based on two types of carriers, holes and electrons, unipolar transistors operate with only one type of charge, holes or electrons. They have three electrodes: the source (S), the drain (D) and a control electrode called gate (G).

The operation of the field-effect transistor (FET) can be explained in terms of only majority-carrier (one-polarity) charge flow; the transistor is therefore called unipolar. Two kinds of field-effect devices are widely used: the junction field-effect transistor (JFET) and the metal-oxide-semiconductor field-effect transistor (MOSFET).

2. Partie I : Transistor J-FET

P type substrate (Gate) heavily doped (P^+) is deposited: A weakly doped N zone which constitutes the channel, two heavily doped N zones (N^+) which constitute input (Source) and output terminals of the channel (Drain). If we reverse the doping we obtain a P-channel field effect transistor.

 


Figure 1 : Structure of N channel JFET transistor

The JFET transistor is made up of three terminals:

- 1) The source (S) in which injects the carriers of charges into the structure.

2) The drain (D) in which collects the carriers: the drain.

3) The Gate (G) where the control voltage is applied.

2.1. JFET construction and symbols

Conduction is ensured by the passage of charge carriers from source (S) to drain (D) through the channel between the gate (G) elements.

The transistor can be an N-channel device (conduction by electrons) or an P-channel device (conduction by holes);

The following figures illustrate the basic structure of a JFET transistor.

 
 


Figure 2 : N channel JFET

 
 


Figure 3 : P channel JFET

- ✓ If we put an FET under a V_{GS} voltage, we expand or narrow the channel allowing the circulation of carriers between the drain and the source.
- ✓ We speak of an N channel when the doping of this channel is of type N, and of a P channel in the opposite case.
- ✓ Depending on the type of channel, the V_{GS} sign allows to modify its size.

2.2. Voltages and currents

The JFET transistor has three terminals, three currents and three voltages must be defined:

For an N-channel JFET in normal operation:

- 1) The V_{DS} voltage is positive
- 2) The V_{GS} voltage is negative or weakly positive ($< 0.6\text{ V}$)
- 3) The gate current is almost zero $I_G = 0$. Law of nodes: $I_S = I_D$
- 4) Current enters the transistor through the drain (I_D)
- 5) The current leaves the transistor through the source (I_S)

2.3. Fonctioning fo N-Channel JFET

The N-channel field effect transistor is controlled by applying a Gate Source voltage V_{GS} :

- Negative V_{GS} in the case of an N type, and the drain is positively polarized with respect to the source. Positive V_{GS} in the case of type P.
- The drain-source space receives a bias voltage (V_{DS} voltage)

The JFET conducts if $V_{GS} \geq V_P$, V_P is the pinch-off voltage (closed channel, $I_D=0$), it is a negative reverse voltage.

3. The characteristics of N-channel JFET

In this section we will deal with the characteristics of a JFET transistor:

3.1. Output characteristic $I_D=f(V_{DS})$ with V_{GS} constant

When we set for example $V_{GS}=0$, the channel N behaves like a resistor R_D and we see that the drain current I_D increases with the drain source voltage V_{DS} in a practically linear manner up to a value equal to V_P (pinch voltage).

From this voltage (pinch voltage) the current I_D no longer varies and keeps a practically constant value equal to I_{DSS} (max current for a JFET). In this case we say that the saturation range has been reached.

Note: It should be noted that the V_{DS} voltage cannot increase indefinitely without the risk of destroying the transistor. We therefore limit V_{DS} to a maximum voltage which we note $V_{DS\text{ max}}$.

 


Figure 4 : N channel JFET Biasing circuit

 


Figure 5 : Output characteristic $I_D=f(V_{DS})$

- The active region of the JFET is located between voltages V_P and V_{DSmax} .
- V_P : pinch voltage (closed channel $I_D=0$ for $V_{GS}=V_P$). V_P is the value of V_{DS} for which the drain current becomes constant and is always measured when $V_{GS}=0$
- V_{GSoff} and V_P are always equal but in opposite sign
- I_{DSS} represents the current between the drain and the source when the gate is connected to the source (short-circuited gate); This is the maximum current that an JFET can produce.

The Figure above defines the four working areas of a JFET:

1. The Ohmic region: When V_{DS} is very small, the JFET functions as a controlled resistor.
2. The active or saturation region:
 - It is in this area that we will use the FET.
 - The JFET acts as a current source controlled by the gate voltage.
3. The breakdown region: The voltage V_{DS} between the drain and the source is high enough to create a breakdown of the resistive channel. The current I_D then increases in an uncontrolled manner.

3.2. Transfer characteristic $I_D=f(V_{GS})$ with V_{DS} constant

The evolution of the drain current I_D as a function of V_{GS} with $V_{DS} = \text{Cste}$ is represented by Figure 6.

The defining equation of this curve is given by:

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_{GSoff}} \right]^2$$

I_{DSS} : Drain Source current for $V_{GS}=0$.

$$V_{GSoff} = -V_p$$

 


Figure 6 : Transfer characteristic $I_D = f(V_{GS})$

From the curve $I_D=f(V_{GS})$, we define what we call the slope or the transconductance g_m (AC) of a field effect transistor.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{dI_D}{dV_{GS}}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GSoff}} \right) \text{ with}$$

$$g_{m0} = -2I_{DSS}/V_{GSoff}$$

g_{m0} : Transconductance at $V_{GS}=0$

3. Static study of a JFET transistor

3.1. Static load line and rest point

- 1) The static load line is expressed by: $I_D=f(V_{DS})$.
- 2) The operating point defined by the point of intersection between the static load line and the characteristic.

3) The operating point (rest) is fixed by an ordinate I_{DQ} , and an abscissa V_{DSQ} .

3.2. Bias circuits of a JFET transistor

In the same way as for the bipolar transistor we must choose an operating point before defining the small signal parameters because these will be a function of this operating point. To do this, the transistor must be polarized.

3.2.1. Automatic biasing

In the case of automatic polarization, only one source is applied (V_{DD}) as shown in the figure below:

 


Figure 7 : Automatique polarisation of JFET


Required work: write the equation of the load line.

➤ load Line equation:

$$V_{DD} - V_{DS} = R_D I_D - R_S I_D$$

$$I_S = I_D \Rightarrow I_D = (V_{DD} - V_{DS}) / (R_S + R_D)$$

 
The operating point is described by the point Q, and shown schematically on the graph.



➤ Attack line equation :

$$V_{GS} = -R_G I_G - R_S I_S \quad (I_G \approx 0) \Rightarrow$$

$$I_D = -V_{GS}/R_S$$

 

3.2.1. Biasing by two independent sources

In this type of polarization two voltage generators are applied; one at the grid and the other at the Drain terminal.

 


Figure 8 : Biasing of a JFET by two independent sources

The load line can be written as follow:

$$I_D = (V_{DD} - V_{DS})/R_D$$

3.2.2. Biasing with a single voltage source

In this type of polarization a single source is applied at the gate and the drain.

 


Figure 9 : Polarisation d'un JFET

The load line can be written as follow : $ID = (VDD - VDS)/(RD + RS)$

4. Equivalent diagram of a small signal JFET at low frequency

The equivalent diagram of the JFET in a small signal regime and at low frequency is given in the following figure:

 


Figure 10 : Low frequency equivalent model of a JFET

gm : the transconductance of the transistor, is the slope of the transfer characteristic $ID (VGS)$.

The exploitation of the equivalent diagram of the transistor will make it possible to calculate the following quantities:

- Voltage amplification $A_v = \frac{v_2}{v_1}$
- Input Impedance $Z_e = \frac{v_1}{i_1}$
- Output Impedance $Z_s = \frac{v_2}{i_2}$

Note :

In the dynamic regime:

- ✓ The capacitors C are replaced by short circuits at the signal frequency.
- ✓ The DC voltage source is replaced by earthing.

5.3. Amplificateurs à FET à faible signaux

Comme pour le transistor bipolaire, il existe trois montages types pour le TEC. L'étude des performances de ces montages se fait par l'évaluation du gain en tension, et des impédances d'entrée et de sortie.

5.3. Low-signal FET amplifiers

As with the bipolar transistor, there are three typical configurations for the JFET transistor. The performance of these circuits is studied by evaluating the voltage gain, and the input and output impedances.

5.3.1. Common Source FET Amplifier

We consider the study the common source FET amplifier given in the figure below:


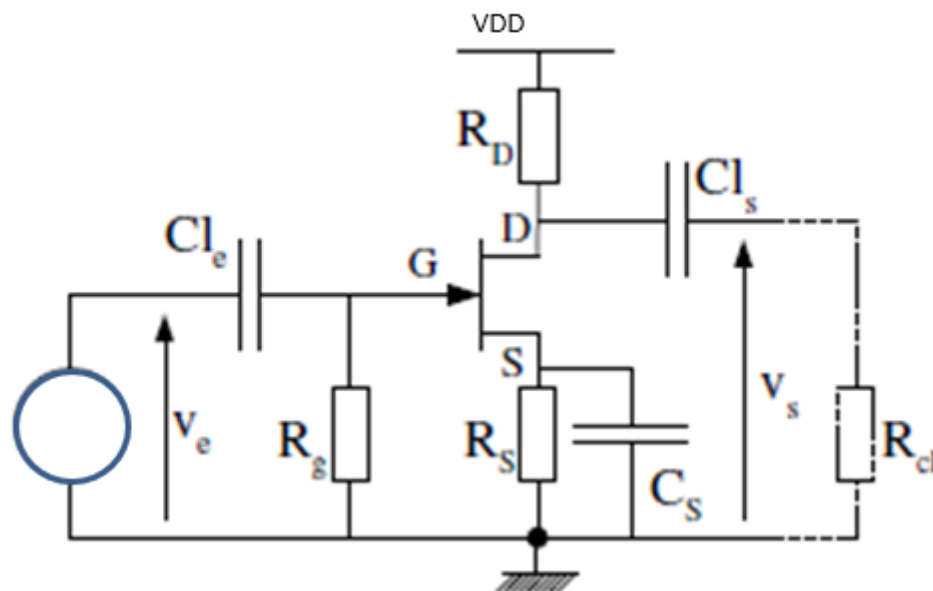


Figure 11 :Common source FET

Work required: Calculate A_v , Z_e and Z_s .

1) Dynamic study

 

2) Voltage Amplification $A_v = ?$

we pose : $R_d = R_D // R_L$

$$i_d = g_m V_{gs} \quad (1)$$

$$v_e = v_{gs} \quad (2)$$

$$v_s = -r_d \cdot i_d \quad (3)$$

We replace equation (1) in equation (3) $\Rightarrow V_s = -r_d \cdot g_m \cdot V_{gs}$

(4)

$$\frac{4}{1} \text{ gives } A_v = -r_d \cdot g_m$$

3) Input impedance $R_e = \frac{v_e}{i_e}$

$$V_e = R_g \cdot i_e \Rightarrow \frac{v_e}{i_e} = R_g$$


4) Output impedance $R_s = ?$

For that it is necessary :

- Remove the R_L load
- Cancel input generator eg (DC all voltage sources)

Apply a voltage generator instead of R_L

Calculate $Z_s = V_s / i_s$

 

$$R_s = \frac{V_s}{i_s} = R_D$$

5.3.2. Common Drain FET Amplifier

We consider the following common drain FET amplifier:


 


Figure 12 : Common drain FET

Work : Calculate A_v , Z_e et Z_s .

 - 1) The equivalent alternative diagram is given in the figure bellow :



Required work : Calculate A_v , R_e et R_s .

1) Voltage gain $A_v = \frac{V_s}{V_e}$

We pose : $r_s = R_s // R_L$

$$V_e = V_{gs} + V_s \quad (1)$$

$$V_s = r_s g_m V_{gs} \quad (2)$$

We replace equation (2) in equation (1), we obtain :

$$V_e = V_{gs}(1 + r_s g_m) \quad (3)$$

(2)/(3) give : $A_v = \frac{g_m r_s}{1 + r_s g_m}$

2) Input impedance $R_e = \frac{V_e}{i_e}$

$$R_e = R_G$$

3) Output impedance $R_s = \frac{v_s}{i_s}$


$$V_s = (i_s + g_m v_{gs}) R_s \quad (4)$$

$$V_s = -V_{gs} \quad (5)$$

We replace equation (5) in equation (4), we obtain :

$$i_s - g_m V_s - \frac{V_s}{R_s} = 0 \Rightarrow i_s = v_s \left(g_m + \frac{1}{R_s} \right)$$
 
$$\Rightarrow R_s = \frac{1}{g_m + \frac{1}{R_s}}$$



5.3.3. Common Gate FET Amplifier

Consider the following common gate FET amplifier:


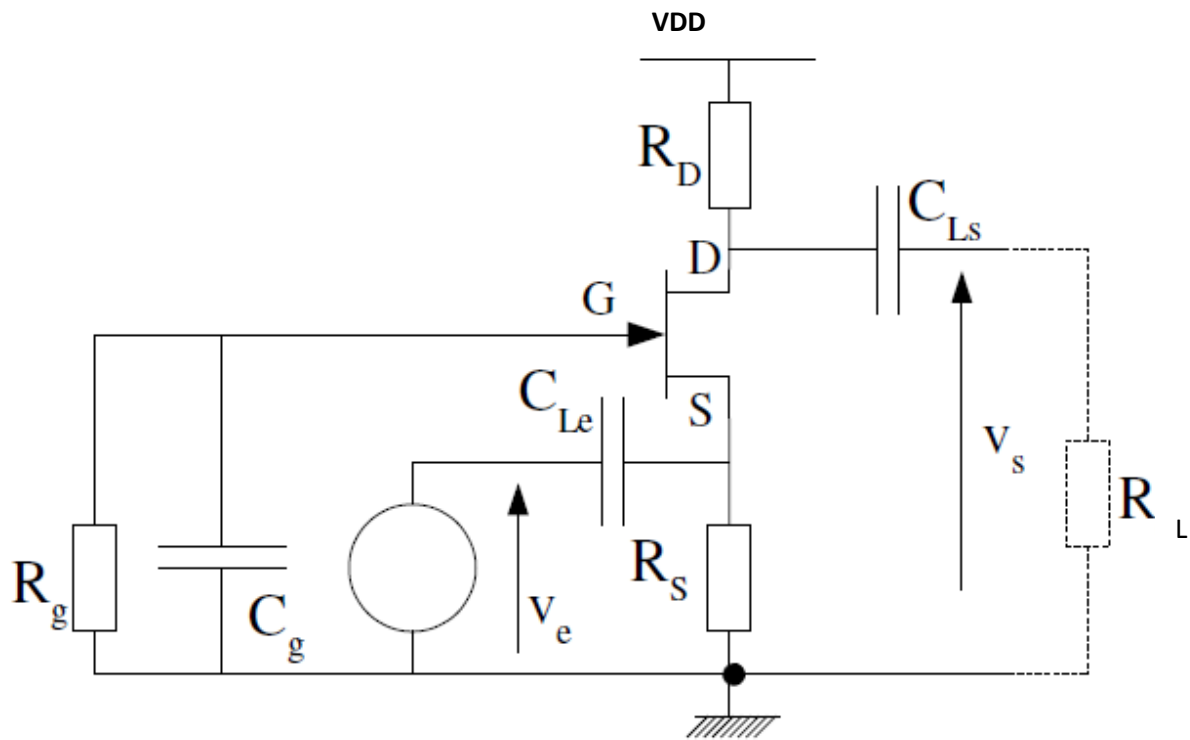


Figure 13 : Common Gate FET Amplifier

Required work : Calculate A_v , Z_e et Z_s .

 1. Equivalent scheme of the common gate FET in dynamics



We have: $V_s = -V_{gs}$

1) Voltage amplification

we pose : $r_d = R_D // R_L$

we have :

$$v_e = -v_{gs} \quad (1)$$

$$V_s = -r_d g_m V_{gs} \quad (2)$$

Equation 1/equation 2, on obtient : $\frac{V_s}{V_e} = \frac{V_s}{V_{gs}} = r_d g_m$

$$A_V = g_m r_d$$

1) Input impedance $R_e = \frac{V_e}{i_e}$

$$V_e = R_s(i_e + g_m V_{gs})$$

$$V_e = -V_{gs}$$

$$i_e + V_{gs} \left(g_m + \frac{1}{R_s} \right) = 0$$

$$i_e = -V_{gs} \left(g_m + \frac{1}{R_s} \right) \rightarrow R_e = \frac{V_e}{i_e} = \frac{1}{g_m + \frac{1}{R_s}}$$

2) Output impedance

- Disconnect the load R_L
- Cancel the voltage generator eg (we short-circuit the voltage sources)
- Place the voltage generator in the place of R_L

$$v_{gs} = 0 \Rightarrow g_m v_{gs} = 0$$

$$V_s = R_D i_s \Rightarrow R_s = \frac{V_s}{i_s} = R_D$$

