

4.5 Three phase controlled rectifier

Three phase converters are 3-phase controlled rectifiers which are used to convert ac input power supply into dc output power across the load. The features of 3-phase controlled rectifiers are;

- Operate from 3 phase ac supply voltage
- They provide higher dc output voltage and higher dc output power.
- Higher output voltage ripple frequency.
- Filtering requirements are simplified for smoothing out load voltage and load current.
- Three phase controlled rectifiers are extensively used in high power variable speed industrial dc drives.

4.5.1 Three phase half wave controlled rectifier with R load

The thyristor will conduct (ON state), when the anode-to-cathode voltage is positive and a firing current pulse is applied to the gate terminal. Delaying the firing pulse by an angle α controls the load voltage.

When the load is resistive, current $i_o(\omega t)$ has the same waveform of the load voltage. As the load becomes more and more inductive, the current flattens and finally becomes constant. The thyristor goes to the non-conducting condition (OFF state) when the following thyristor is switched ON, or the current, tries to reach a negative value.

For resistive load

- $0^\circ \leq \alpha \leq 30^\circ$, output voltage is continuous.
- $30^\circ \leq \alpha \leq 120^\circ$, output voltage is discontinuous and has some intervals in which output voltage is zero.
- $\alpha > 150^\circ$, output voltage is zero.

1-Continuous case $\alpha \leq 30^\circ$

Three single phase half-wave converters are connected together to form a three phase half-wave converter as shown in the figure (7.4).

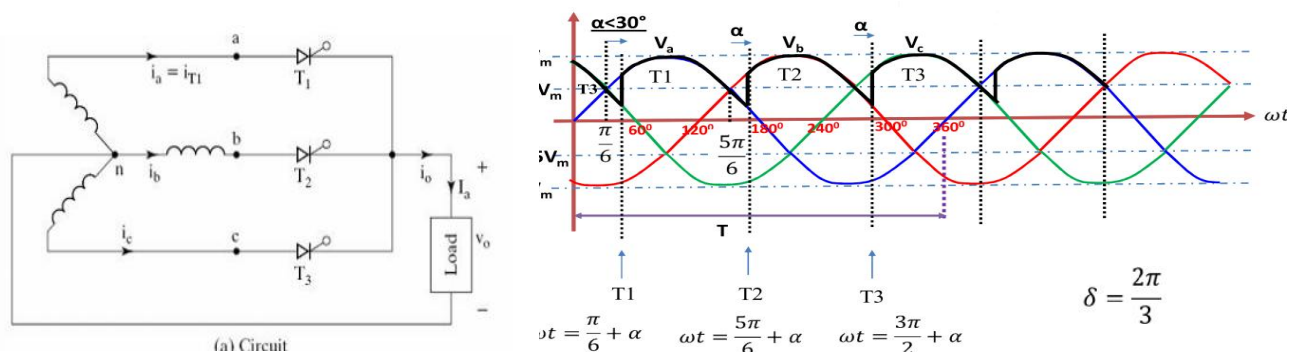



Fig4.7 three phase thyristor half wave rectifier (a) circuit ,(b) output voltage Continuous waveform

The average and rms load voltages are

$$V_{dc} = \frac{3V_m}{2\pi} \left[\int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} \sin \omega t \cdot d(\omega t) \right]$$

$$V_{dc} = \frac{3V_m}{2\pi} \left[(-\cos \omega t) \Big/_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} \right]$$
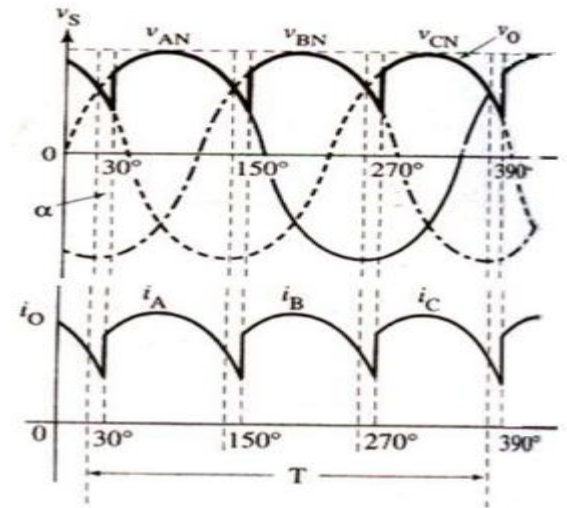
$$V_{dc} = \frac{3V_m}{2\pi} \left[-\cos \left(\frac{5\pi}{6} + \alpha \right) + \cos \left(\frac{\pi}{6} + \alpha \right) \right]$$



Waveforms of three phase HWSCR Continuous Mode with R load

Note from the trigonometric relationship

$$\cos(A+B) = (\cos A \cdot \cos B - \sin A \cdot \sin B)$$

$$V_{dc} = \frac{3V_m}{2\pi} \left[-\cos \left(\frac{5\pi}{6} \right) \cos(\alpha) + \sin \left(\frac{5\pi}{6} \right) \sin(\alpha) \right. \\ \left. + \cos \left(\frac{\pi}{6} \right) \cdot \cos(\alpha) - \sin \left(\frac{\pi}{6} \right) \sin(\alpha) \right]$$

$$V_{dc} = \frac{3V_m}{2\pi} \left[-\cos(150^\circ) \cos(\alpha) + \sin(150^\circ) \sin(\alpha) \right. \\ \left. + \cos(30^\circ) \cdot \cos(\alpha) - \sin(30^\circ) \sin(\alpha) \right]$$

$$V_{dc} = \frac{3V_m}{2\pi} \left[-\cos(180^\circ - 30^\circ) \cos(\alpha) + \sin(180^\circ - 30^\circ) \sin(\alpha) \right. \\ \left. + \cos(30^\circ) \cdot \cos(\alpha) - \sin(30^\circ) \sin(\alpha) \right]$$

Note: $\cos(180^\circ - 30^\circ) = -\cos(30^\circ)$

$\sin(180^\circ - 30^\circ) = \sin(30^\circ)$

$$\therefore V_{dc} = \frac{3V_m}{2\pi} \left[+\cos(30^\circ) \cos(\alpha) + \sin(30^\circ) \sin(\alpha) \right. \\ \left. + \cos(30^\circ) \cdot \cos(\alpha) - \sin(30^\circ) \sin(\alpha) \right]$$

$$V_{dc} = \frac{3V_m}{2\pi} [2 \cos(30^\circ) \cos(\alpha)]$$

$$V_{dc} = \frac{3V_m}{2\pi} \left[2 \times \frac{\sqrt{3}}{2} \cos(\alpha) \right]$$

$$V_{dc} = \frac{3V_m}{2\pi} [\sqrt{3} \cos(\alpha)] = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

$$V_{dc} = \frac{3V_{Lm}}{2\pi} \cos(\alpha)$$

Where $V_{Lm} = \sqrt{3}V_m = \text{Max. line to line supply voltage}$

The maximum average or dc output voltage is obtained at a delay angle $\alpha = 0$ and is given by

$$V_{dc(max)} = V_{dm} = \frac{3\sqrt{3} V_m}{2\pi}$$

Where V_m is the peak phase voltage.

And the normalized average output voltage is

$$V_{dcn} = V_n = \frac{V_{dc}}{V_{dm}} = \cos \alpha$$

The rms value of output voltage is found by using the equation

$$V_{O(RMS)} = \left[\frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m^2 \sin^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$

and we obtain

$$V_{O(RMS)} = \sqrt{3}V_m \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

In the case of a three-phase half wave controlled rectifier with resistive load, the thyristor T1 is triggered at $\omega t = (30^\circ + \alpha)$ and T1 conducts up to $\omega t = 180^\circ$. When the phase supply voltage decreases to zero, the load current falls to zero and the thyristor T1 turns off. Thus T1 conducts from $\omega t = (30^\circ + \alpha)$ to (180°) .

2- Discontinuous case $\alpha \geq 30^\circ$


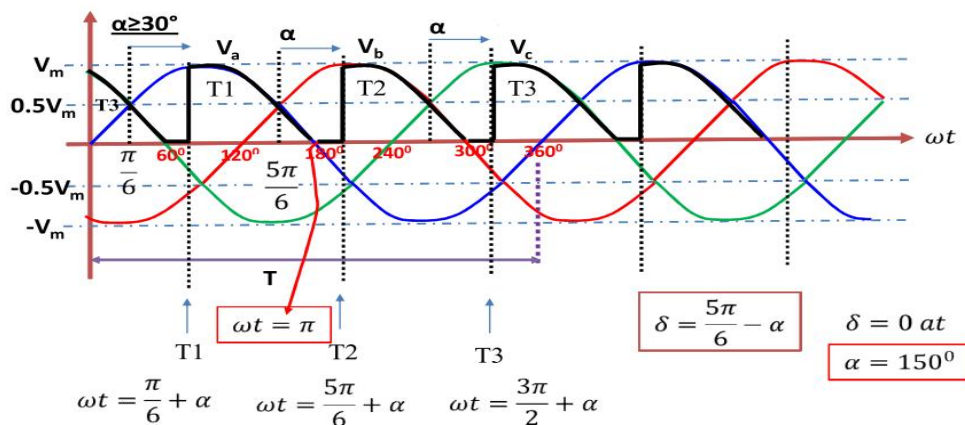


Fig4.8 Output voltage of a Three phase half wave controlled rectifier with R load
(Discontinuous case $\alpha \geq 30^\circ$)

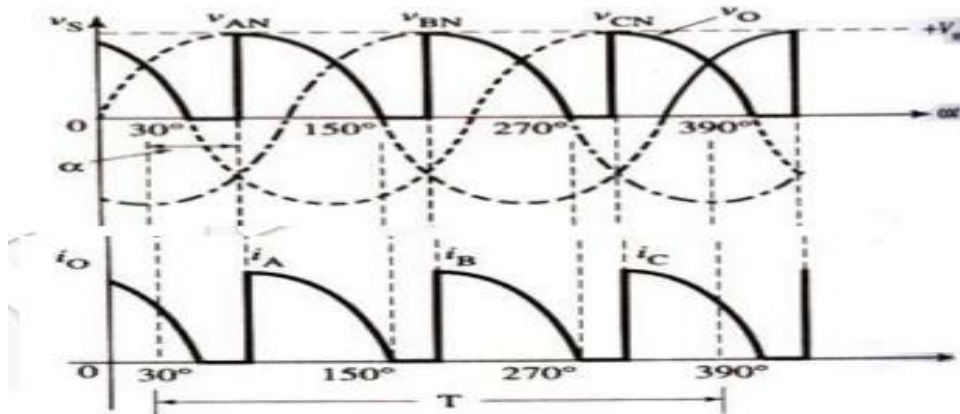

Waveforms of three phase HWSCR discontinuous Mode with R load


The average output voltage is given by;

$$V_{dc} = \frac{3V_{mp}}{2\pi} \left[\int_{\alpha+30^\circ}^{180^\circ} \sin \omega t. d(\omega t) \right] = \frac{3V_{mp}}{2\pi} [1 + \cos(\alpha + 30^\circ)] \quad (4.28)$$

The RMS output voltage is given by;

$$V_{or} = \left[\frac{3}{2\pi} \int_{\alpha+\pi/6}^{\pi} V_{mp}^2 \sin^2 \omega t. d(\omega t) \right]^{1/2} = \frac{\sqrt{3} \cdot V_{mp}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]^{1/2} \quad (4.29)$$

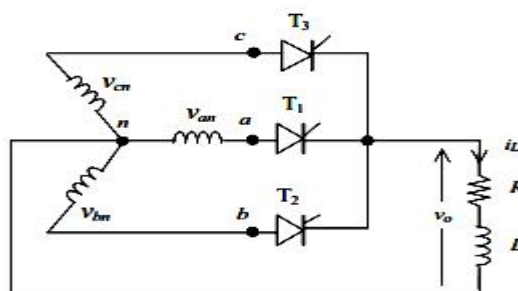4.5.2 Three phase half wave controlled rectifier with RL load



Three -Phase HWSCR With RL Load

- For firing angle $\alpha < 30^\circ$ the same equations for $V_o(dc)$ and $V_o(rms)$ when $\alpha < 30^\circ$ with R Load.
- For firing angle $\alpha = 30^\circ$ the same equations for $V_o(dc)$ and $V_o(rms)$ when $\alpha > 30$ with R Load.
- For $30^\circ < \alpha < 90^\circ$, $V_o(dc)$ and $V_o(rms)$ are different based on new " ωt " range.

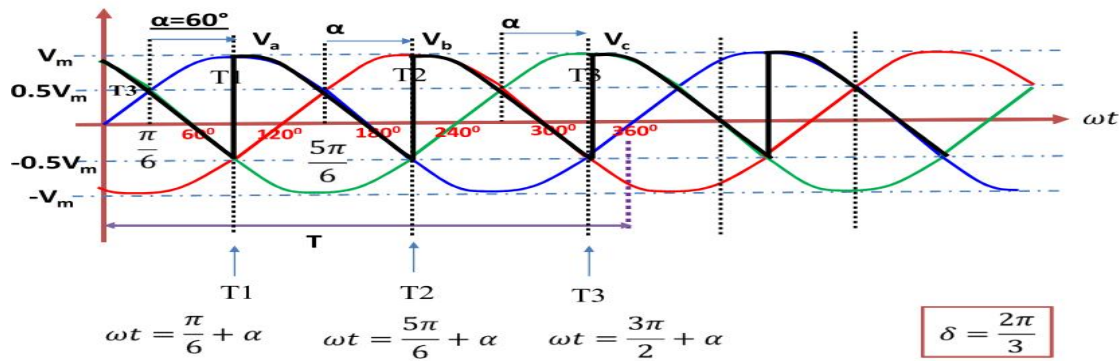


Fig4.9 Output voltage of a Three phase half wave controlled rectifier with RL load
case $\alpha \geq 30^\circ$, $\alpha = 60^\circ$;


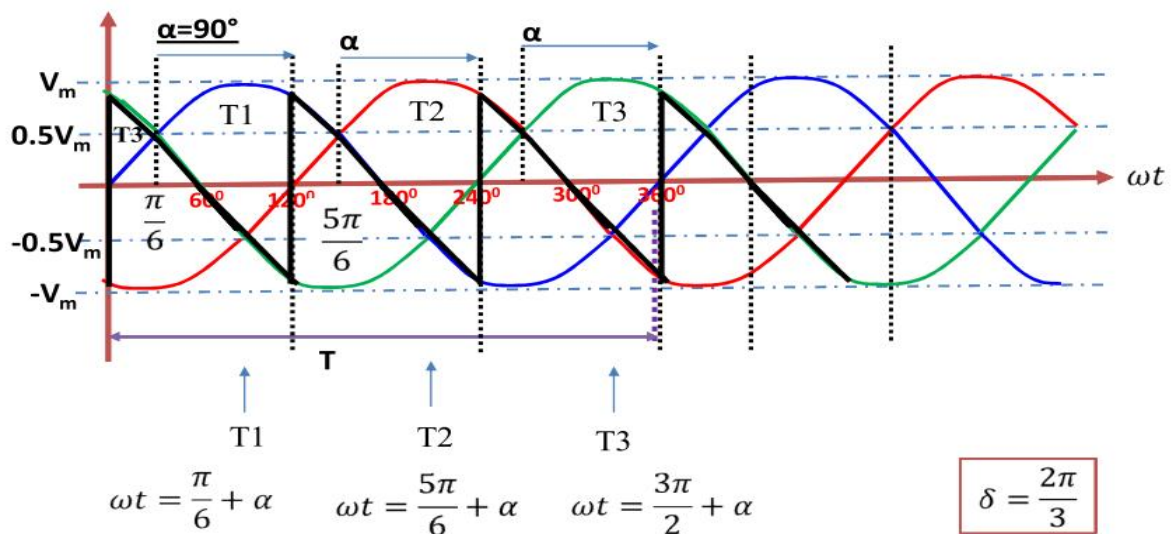


Fig4.10 Output voltage of a Three phase half wave controlled rectifier with RL load
case $\alpha \geq 30^\circ$, $\alpha = 90^\circ$;


- Average voltage at $\alpha = 90^\circ$; $V_{o(dc)} = 0V$.
- In a three phase half wave controlled rectifier with RL load and freewheeling diode, $V_o(dc)$ will be look like when R-load used for $\alpha \geq 30^\circ$.
- Beyond $\alpha > 90^\circ$ or between $90^\circ < \alpha < 180^\circ$, $V_o(dc)$ is negative, three phase 3-pulse converter operates as a line commutated inverter. for example if $\alpha = 120^\circ$, the

$$V_{o(dc)} = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha) \quad (4.29)$$
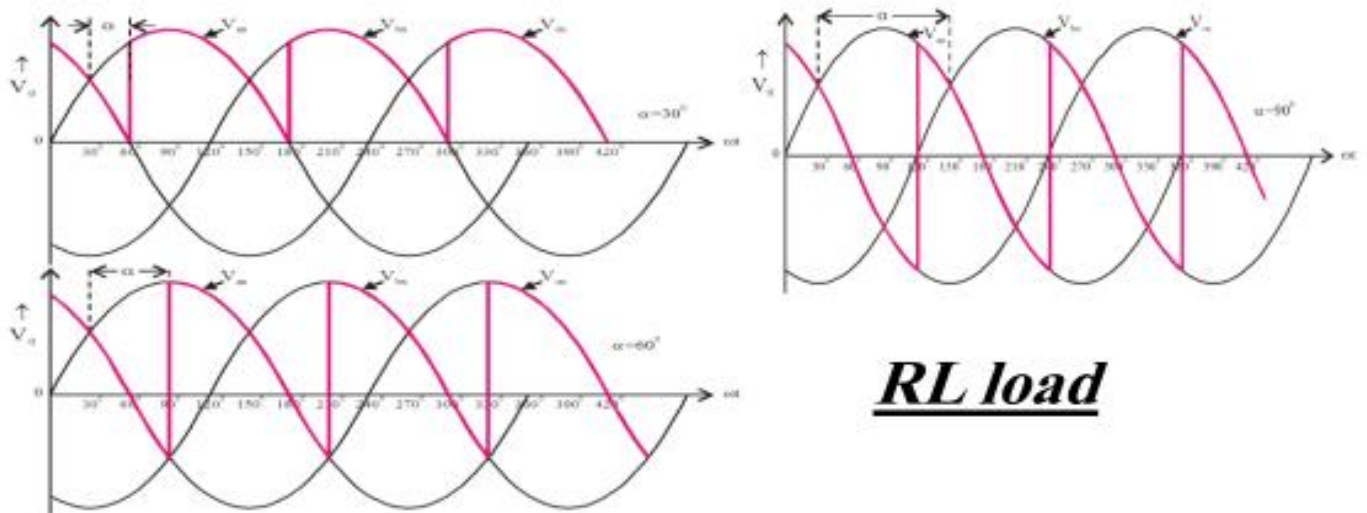
$$V_{o(dc)} = 0.827 * V_m * \cos(120^\circ) = -0.414 V_m$$




RL load

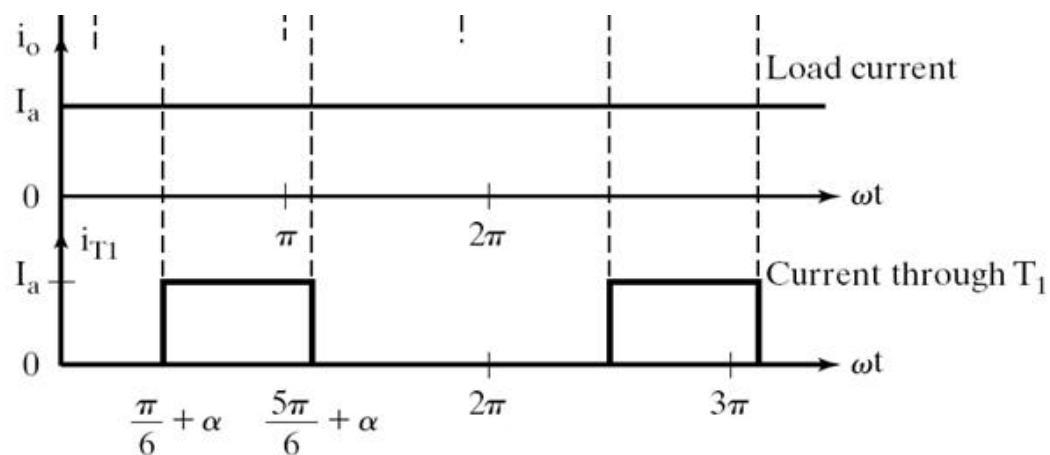


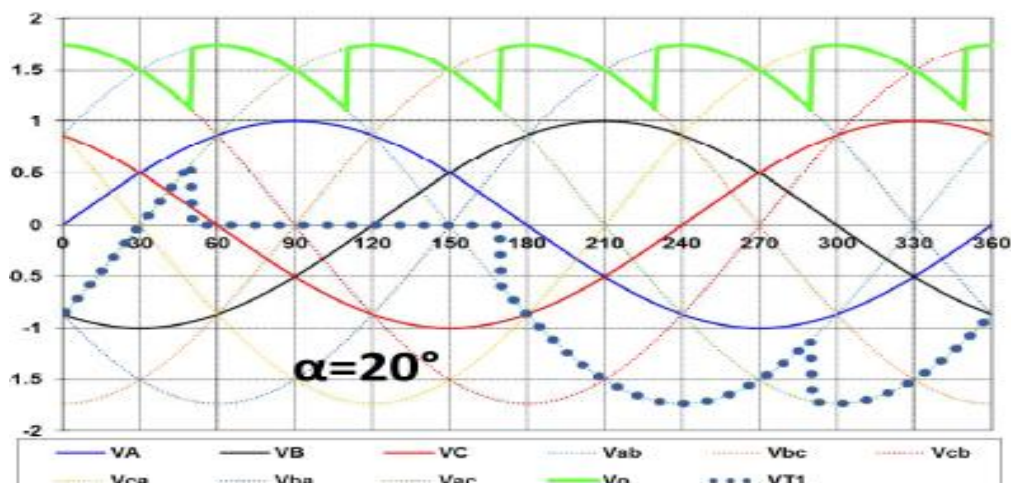4.5.3 Three phase full wave controlled rectifier with R load

- For any $\alpha \leq 60^\circ$ the output current continues and no zero voltage is appear in the output voltage.



- For $\alpha > 60^\circ$;

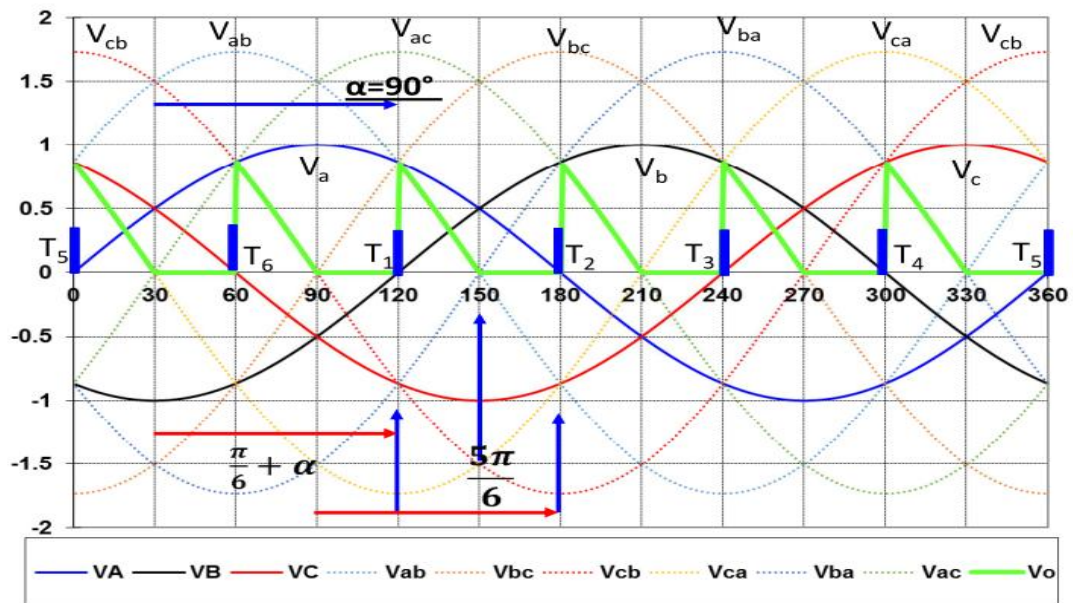

the average output voltage is


$$V_{o(av)} = \frac{1}{\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \sqrt{3} V_m \sin\left(\omega t + \frac{\pi}{6}\right) d\omega t$$

$$V_{o(av)} = \frac{3\sqrt{3} V_m}{\pi} \left[1 + \cos\left(\frac{\pi}{3} + \alpha\right) \right]$$


The RMS output voltage is $V_{or} = \frac{V_{ml}}{2\sqrt{\pi}} \sqrt{(4\pi - 6\alpha + 3\cos(\frac{\pi}{6} + 2\alpha))}$

4.5.4 Three phase bridge converter with RL load:

$\alpha \leq 60^\circ$

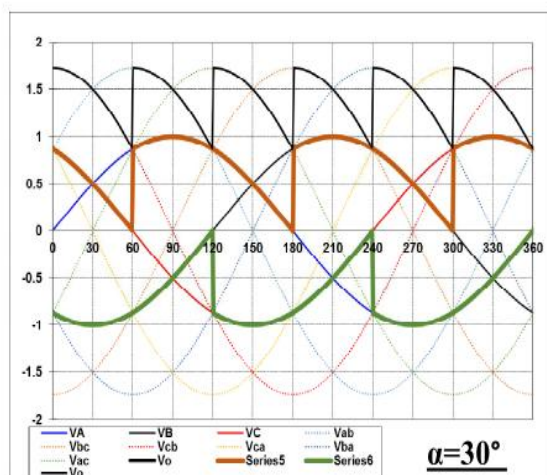


RL-Load

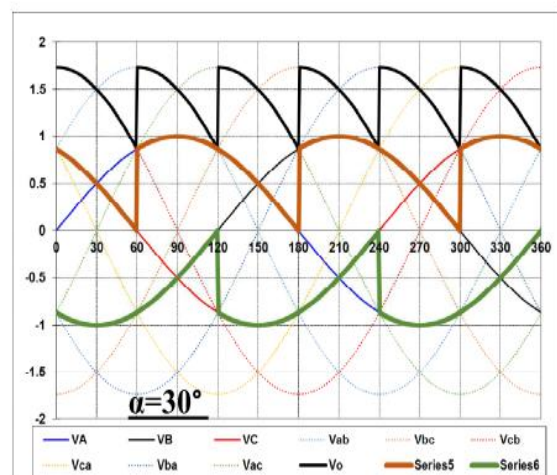

R-Load

For heavy inductive load, the RMS and DC output voltage equation are same one shown in R-Load for $\alpha \leq 60^\circ$.

- For $\alpha > 60^\circ$;

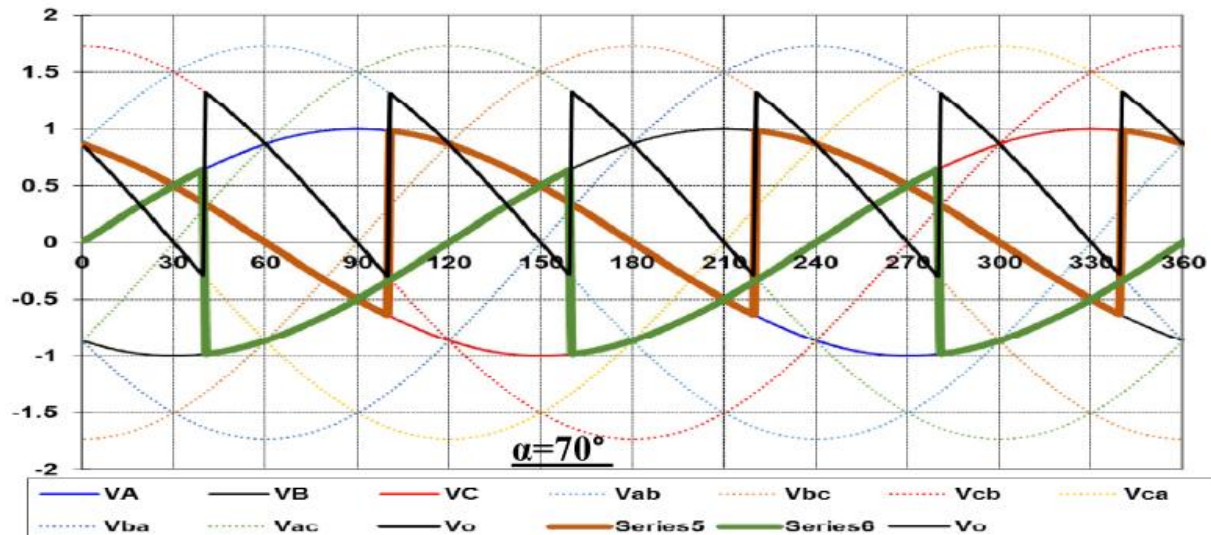

Due to the magnetic field a high voltage is induced across the inductor in the direction required to keep the current flowing. This results in negative voltage appearing across a RL load.

- At $\alpha=90^\circ$ the DC output voltage is equal to zero.
- at $\alpha=120^\circ$ the output voltage is negative

Worked examples:

Example 2: a single phase bridge rectifier has load of $R=15\ \Omega$ and, $V_s=220 \sin 314 t$ and unity transformer ratio. If it is required to obtain an average output voltage of 70% of the maximum possible output voltage, calculate:- (a) The delay angle α , (b) The efficiency, (c) Ripple factor of output voltage (d) The peak inverse voltage (PIV) of one thyristor.

Solution:

$$V_n = \frac{V_{dc}}{V_{dm}} = 0.5 (1 + \cos \alpha) = 0.7, \text{ then, } \alpha = 66.42^\circ$$

$$V_m = 220, \text{ then, } V_{dc} = 0.7 * V_{dm} = 0.7 * \frac{2 V_m}{\pi} = 98.04 \text{ V}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{98.04}{15} = 6.536 \text{ A}$$

$$V_{rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{\sin(2\alpha)}{2}}$$

$$\alpha = 66.42^\circ \quad V_{rms} = 134.638 \text{ V. Then, } I_{rms} = 134.638 / 15 = 8.976 \text{ A}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{98.04 * 6.536}{134.638 * 8.976} = 53.04\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{134.638}{98.04} = 1.3733$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.3733^2 - 1} = 0.9413$$

The PIV is V_m

Example 03 : A controlled full-wave bridge rectifier has pure DC load current of 50 A and, $V_s = 220 \sin 314 t$ and unity transformer ratio. If it is required to obtain an average output voltage of 70% of the maximum possible output voltage, calculate:- (a) The delay angle α , (b) The efficiency, (c) Ripple factor (d) The peak inverse voltage (PIV) of the thyristor.

Solution:

$$V_n = \frac{V_{dc}}{V_{dm}} = \cos \alpha = 0.7 \quad \text{then, } \alpha = 45.5731^\circ = 0.7954$$

$$V_m = 220, \quad V_{dc} = 0.7 * V_{dm} = 0.7 * 2 V_m / \pi = 98.04 \text{ V}, \quad V_{rms} = V_m / \sqrt{2}$$

$$\text{At } \alpha = 45.5731^\circ \quad V_{rms} = 155.563 \text{ V. Then, } I_{rms} = 50 \text{ A}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{98.04 * 50}{155.563 * 50} = 63.02\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{155.563}{98.04} = 1.587$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.587^2 - 1} = 1.23195$$

Example 04: Three-phase full-wave controlled rectifier is connected to 380 V, 50 Hz supply to feed a load of 10Ω pure resistance. If it is required to get 400 V DC output voltage, calculate the following: (a) The firing angle, α (b) The rectification efficiency (c) PIV of the thyristors.

Solution:

$$V_{dc} = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha = \frac{3\sqrt{3}}{R} * \frac{\sqrt{2}}{\sqrt{3}} * 380 \cos \alpha = 400V .$$

$$\text{Then } \alpha = 38.79^\circ, \quad I_{dc} = \frac{V_{dc}}{R} = \frac{400}{10} = 40A$$

From (3.84) the rms value of the output voltage is:

$$V_{rms} = \sqrt{3} V_m \sqrt{\left(\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha \right)} = 412.412 V$$

$$\text{Then, } V_{rms} = 412.412 V \quad \text{Then, } I_{rms} = \frac{V_{rms}}{R} = \frac{412.412}{10} = 41.24 A$$

$$\text{Then, } \eta = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} * 100 = \frac{400 * 40}{412.4 * 41.24} * 100 = 94.07\%$$

$$\text{The PIV} = \sqrt{3} V_m = 537.4V$$

Example 05: Solve the previous example if the required dc voltage is 150V.

Solution:

$$V_{dc} = \frac{3\sqrt{3} * \frac{\sqrt{2}}{\sqrt{3}} * 380}{\pi} [1 + \cos(\pi/3 + \alpha)] = 150V \quad \alpha = 73^\circ$$

It is not acceptable result because the above equation valid only for $\alpha \leq 60$

Then we have to use the following expression to get α :

$$V_{dc} = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha = \frac{3\sqrt{3} * \frac{\sqrt{2}}{\sqrt{3}} * 380}{\pi} \cos \alpha = 150V, \quad \alpha = 75.05^\circ$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{150}{10} = 15A$$

The rms value of the output voltage is

$$V_{rms} = \sqrt{3} V_m \sqrt{1 - \frac{3}{4\pi} \left(2\alpha - \cos \left(2\alpha + \frac{\pi}{6} \right) \right)} = \sqrt{3} * \frac{\sqrt{2}}{\sqrt{3}} * 380 * \sqrt{\left(1 - \frac{3}{4\pi} \left(2 * 75.05 * \frac{\pi}{180} - \cos (2 * 75.05 + 30) \right) \right)}$$

$$V_{rms} = 198.075 V$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{198.075}{10} = 19.8075 A \quad \eta = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} * 100 = \frac{150 * 15}{198.075 * 19.81} * 100 = 57.35 \%$$

$$\text{The PIV} = \sqrt{3} V_m = 537.4V$$