

**LABORATORY
EXPERIMENT
NO. 44**

THREE - PHASE CIRCUITS

1. To study the relationship between voltage and current in three-phase circuits.
2. To learn how to make delta and wye connections.
3. To calculate the power in three-phase circuits.

Students tend to approach three-phase circuits with a certain apprehension which is not at all justified. Three-phase circuits, in the majority of cases, are symmetrical. They consist of three identical branches, each of which has the same impedance. Each of these branches can be treated exactly like a single-phase circuit. Consequently, three-phase circuits are not necessarily harder to work with than single-phase circuits.

Three-phase systems are usually connected in either a *delta* or a *wye* configuration. Each of these connections has definite electrical characteristics and the designations *delta* and *wye* are derived from the method of connection.

Power Supply Module (0-220/380V/3φ)	EMS 8829
AC Metering Module (250/250/250V) (500/500/500V)	EMS 8429
AC Metering Module (0.25/0.25/0.25A) (1.5/1.5/1.5A)	EMS 8428
Resistance Module	EMS 8319
Connection Leads	EMS 8941

Caution: High voltages are present in this Laboratory Experiment! Do not make any connections with the power on! The power should be turned off after completing each individual measurement!

- ☐ 1. a) Using your EMS Power Supply and AC Metering Module connect the circuit shown in Fig. 44-1.
- ☐ b) Turn on the power supply and adjust the line-to-neutral voltage (as indicated by the power supply voltmeter) to exactly 220 Vac.



- ☐ e) Calculate the average value of the line-to-line voltage.

$$E_{\text{line-to-line}} = \underline{\hspace{2cm}} V$$

☐ 2. a) Reconnect your three voltmeters in order to measure the voltage from each line-to-neutral.
☐ b) Turn on the power supply and adjust the line-to-neutral voltage (as indicated by the power supply voltmeter) to exactly 220Vac.

☐ c) Measure and record each line-to-neutral voltage.

$$E_{4 \text{ to } N} = \text{_____} \text{ Vac}$$

$$E_{5 \text{ to } N} = \text{_____} \text{ Vac}$$

$$E_{6 \text{ to } N} = \text{_____} \text{ Vac}$$

☐ d) Return the voltage to zero and turn off the power supply.

☐ e) Calculate the average value of the line-to-neutral voltage.

$$E_{\text{line-to-neutral}} = \text{_____} \text{ Vac}$$

☐ 3. a) Calculate the ratio of the average line-to-line voltage to the average line-to-neutral voltage.

$$E_{\text{line-to-line}} / E_{\text{line-to-neutral}} = \text{_____}$$

☐ b) Is this ratio approximately equal to the $\sqrt{3}$ (1.73)? _____

☐ 4. a) Repeat Procedures 1 and 2 but this time measure the voltages from the fixed output terminals of your power supply.

$$E_{1 \text{ to } 2} = \text{_____} \text{ Vac} \quad E_{1 \text{ to } N} = \text{_____} \text{ Vac}$$

$$E_{2 \text{ to } 3} = \text{_____} \text{ Vac} \quad E_{2 \text{ to } N} = \text{_____} \text{ Vac}$$

$$E_{1 \text{ to } 3} = \text{_____} \text{ Vac} \quad E_{3 \text{ to } N} = \text{_____} \text{ Vac}$$

☐ b) Are the fixed line-to-line and the line-to-neutral voltages reasonably equal? _____

☐ c) Is the voltage between any two terminals a single-phase voltage or a three-phase voltage? _____

☐ 5. a) Using your EMS Resistance and AC Metering Modules connect the WYE circuit shown in Fig. 44-2. Use a separate resistance section for each of the loads R_1 , R_2 and R_3 . Do not connect the neutral of the resistance module to the neutral of the power supply.

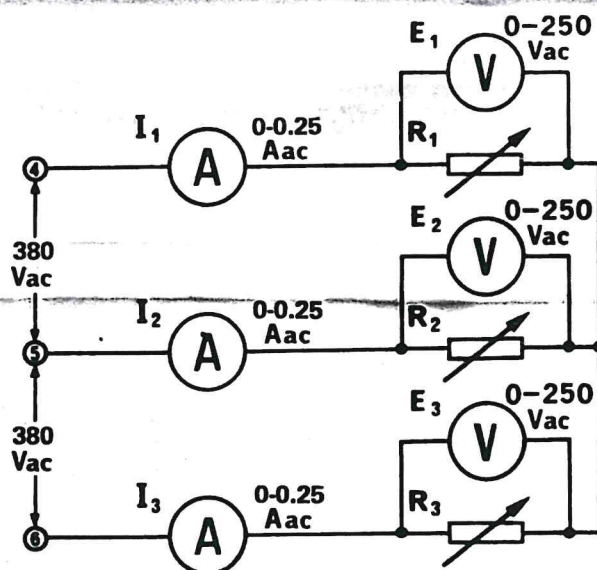


Fig. 44-2

- ☐ b) Set each resistance section to 1100Ω .
- ☐ c) Turn on the power supply and adjust for $380V_{ac}$.
- ☐ d) Measure and record the voltages across, and the currents through, the three load resistances R_1 , R_2 and R_3 .

$$E_1 = \text{_____} V_{ac} \quad I_1 = \text{_____} A_{ac}$$

$$E_2 = \text{_____} V_{ac} \quad I_2 = \text{_____} A_{ac}$$

$$E_3 = \text{_____} V_{ac} \quad I_3 = \text{_____} A_{ac}$$

- ☐ e) Return the voltage to zero and turn off the power supply.
- ☐ f) Are the currents and voltages reasonably well balanced? _____
- ☐ g) Calculate the average value of load voltage.

$$\text{_____} E_{load} = \text{_____} V_{ac}$$

- ☐ h) What is the average value of the line-to-line voltage? (from Procedure 1 (e):

$$E_{line-to-line} = \text{_____} V_{ac}$$

- ☐ i) Calculate the ratio of the average line-to-line voltage to the average load voltage.

$$E_{line-to-line}/E_{load} = \text{_____}$$

- ☐ j) Is this ratio approximately equal to the $\sqrt{3}$ (1.73)? _____

- ☐ k) Calculate the power dissipated by each load resistance.

$$P_1 = \text{_____} W$$

$$P_2 = \text{_____} W$$

$$P_3 = \text{_____} W$$

- ☐ l) Calculate the total three-phase power P_T .

$$P_T = \text{_____} W$$

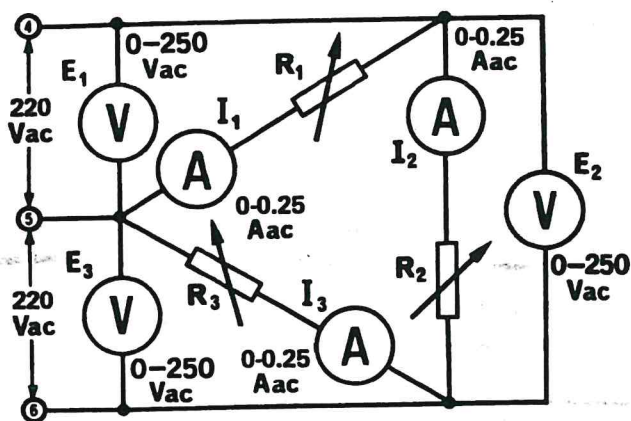


Fig. 44-3

- ☐ 6. a) Connect the DELTA circuit shown in Fig. 44-3.

- ☐ b) Set each resistance section to 1100Ω .
- ☐ c) Turn on the power supply and adjust for $220V_{ac}$ line-to-line.
- ☐ d) Measure and record the voltages across, and the currents through, the three load resistances R_1 , R_2 and R_3 .

$$E_1 = \text{_____} V_{ac} \quad I_1 = \text{_____} A_{ac}$$

$$E_2 = \text{_____} V_{ac} \quad I_2 = \text{_____} A_{ac}$$

$$E_3 = \text{_____} V_{ac} \quad I_3 = \text{_____} A_{ac}$$

- ☐ e) Return the voltage to zero and turn off the power supply.
- ☐ f) Are the currents and voltages reasonably well balanced?
- ☐ g) Calculate the average value of load current.

$$\text{_____} I_{load} = \text{_____} A_{ac}$$

3. In a wye connected circuit, the current is 10 amperes in each resistance load. What is the line current?

4. Three loads each having a resistance of 10 ohms are connected in wye. The total three-phase power is 3000 watts. What is the line-to-line voltage of the power supply?

5. Three resistors each having a resistance of 11 ohms are connected in delta across a 3 ϕ 440 volt line.

a) What is the line current?

b) What is the total three-phase power?

☐ h) Disconnect the three current meters and insert them in series with power supply terminals 4, 5 and 6. Replace the removed current meters with connection leads as shown in Fig. 44-5.

☐ i) Turn on the power supply and adjust for 220 Vac line-to-line.

☐ j) Measure and record the three line currents.

$$I_4 = \text{_____} \text{ Aac}$$

$$I_5 = \text{_____} \text{ Aac}$$

$$I_6 = \text{_____} \text{ Aac}$$

☐ k) Return the voltage to zero and turn off the power supply.

☐ l) Calculate the average value of line current.

$$I_{line} = \text{_____} \text{ Aac}$$

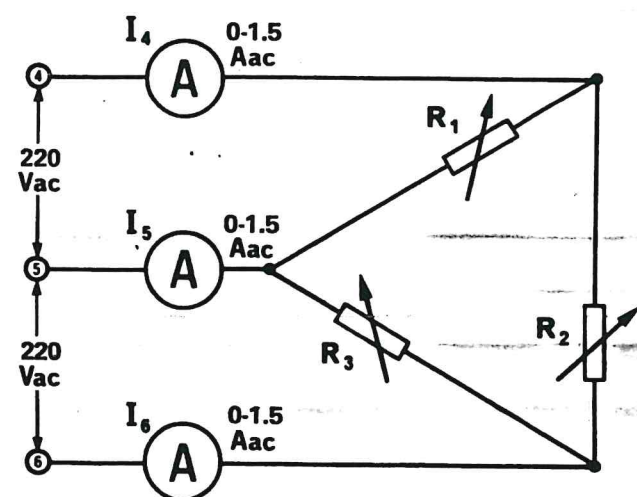


Fig. 44-4

☐ n) Is this ratio approximately equal to $\sqrt{3}$ (1.73)? _____

☐ o) Calculate the power dissipated by each load resistance.

$$P_1 = \text{_____} \text{ W}$$

$$P_2 = \text{_____} \text{ W}$$

$$P_3 = \text{_____} \text{ W}$$

☐ p) Calculate the total three-phase power P_T .

$$P_T = \text{_____} \text{ W}$$

TEST YOUR KNOWLEDGE

1. In a wye connected circuit, if the line-to-line voltage is 346 volts, what is the line-to-neutral voltage?

2. In a delta connected circuit, the current is 20 amperes in each resistance load. What is the line current?

☐ m) Calculate the ratio of the average line current to the average load current.

$$I_{line} / I_{load} = \text{_____}$$