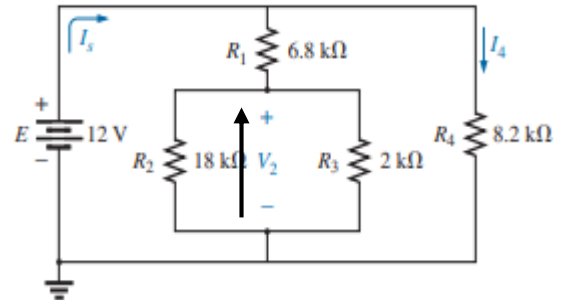


## TD 1

### Exercise 1

For the following network, determine currents  $I_4$ ,  $I_s$  and voltage  $V_2$ .


**Given:**  $R_1=6.8\text{K}\Omega$ ;  $R_2=18\text{K}\Omega$ ;  $R_3=2\text{K}\Omega$ ;  $R_4=8.2\text{K}\Omega$ ;  
 **$E=12\text{V}$ .**


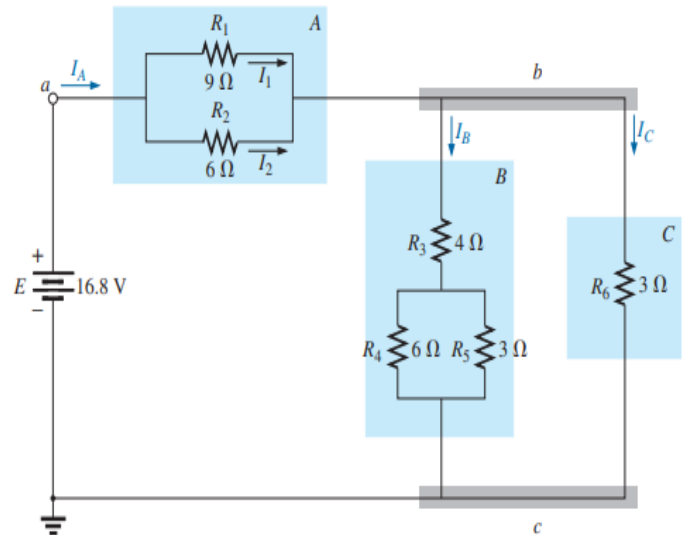
### Exercise 2


Determine all the currents:  $I_a$ ,  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_b$  and  $I_c$  and voltages:  $V_{ab}$  and  $V_{bc}$ .

**Given:**  $R_1=9\Omega$ ;  $R_2=6\Omega$ ;  $R_3=4\Omega$ ;  $R_4=6\Omega$ ;  
 **$R_5=3\Omega$ ;  $R_6=3\Omega$ ;  $E=16.8\text{V}$ .**


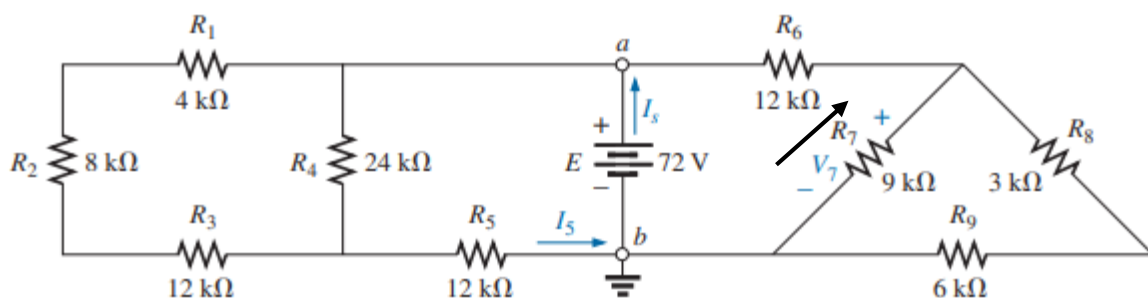
### Exercise 3

Consider the circuit given below, calculate the indicated currents:  $I_5$ ,  $I_s$  and voltage  $V_7$ .



**Given:**  $R_1=4\text{K}\Omega$ ;  $R_2=8\text{K}\Omega$ ;  $R_3=12\text{K}\Omega$ ;  $R_4=24\text{K}\Omega$ ;  $R_5=12\text{K}\Omega$ ;  $R_6=12\text{K}\Omega$ ;  $R_7=9\text{K}\Omega$ ;  $E=72\text{V}$ .


### Exercise 5

Using voltage divider find the voltages:  $V_a$ ?  
 $V_b$ ?  $V_c$ ?

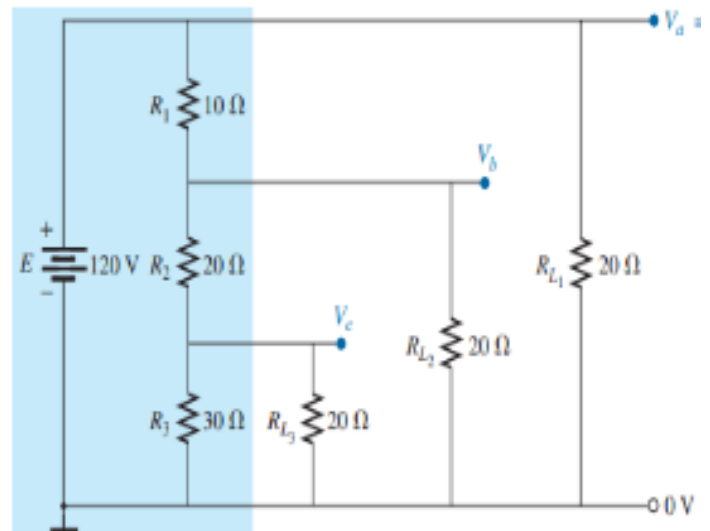**Given:**

$R_1=10\Omega$ ;  $R_2=20\Omega$ ;  $R_3=30\Omega$ ;  $R_{L1}=20\Omega$ ;


$R_{L2}=20\Omega$ ;  $R_{L3}=20\Omega$ ;  $E=120V$ .


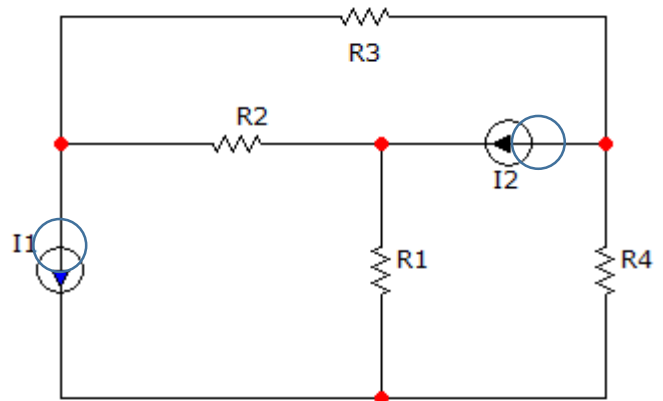
### Exercise 6



In the following network configuration. Find the current and voltage drops through resistor  $R_2$  by using superposition theorem.

**Given:**  $R_1=1\Omega$ ,  $R_2=5\Omega$ ,  $R_3=4\Omega$ ,  $R_4=2\Omega$ ,  
 $I_1=1A$  and  $I_2=2A$


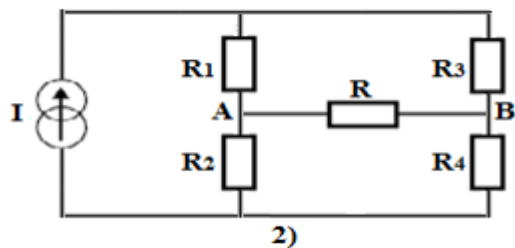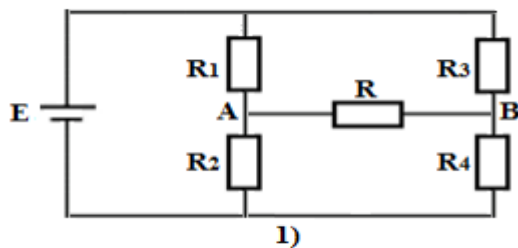
### Exercise 7

For the following two circuits, give the equivalent Thevenin diagram between points A and B.




---
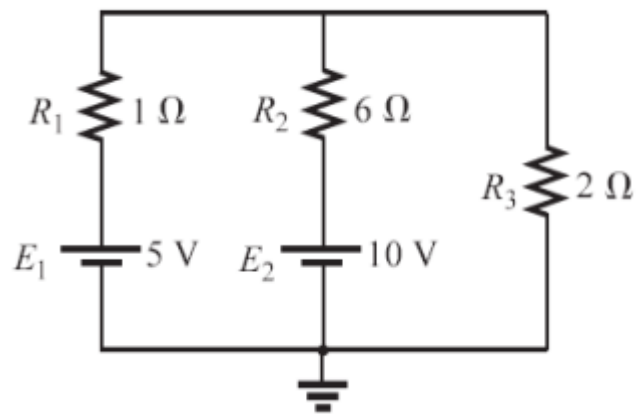
### Exercise 9


Consider the figure bellow, use Millman's theorem to find the current through the  $R_3$  resistor.

**Given:**  $R_1=1\Omega$ ,  $R_2=6\Omega$ ,  $R_3=2\Omega$ ,  $E_1=5V$  and  $E_2=10V$ .


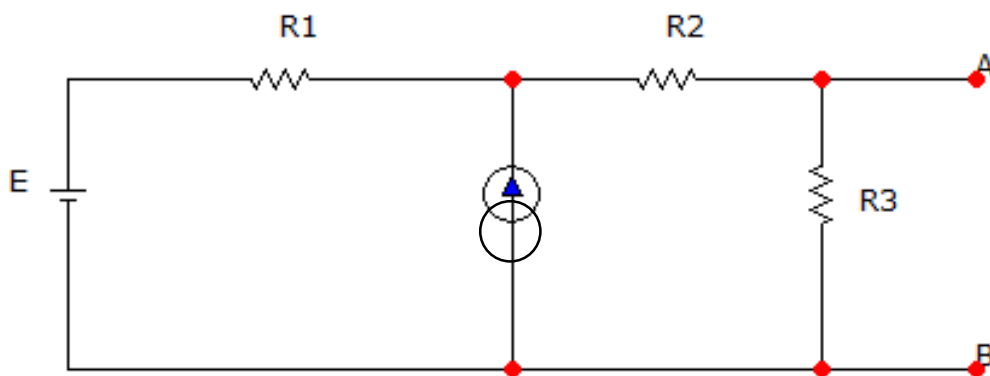
### Exercise 10

Find Norton equivalent circuit at terminals a-b.



**Given:**  $R_1=3\Omega$ ,  $R_2=3\Omega$ ,  $R_3=6\Omega$ ,  $E=15V$  and  $I=4A$


---

## Homework

---
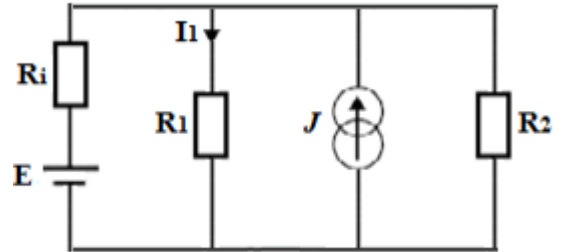
### Exercise 1

Using the superposition theorem, give the expression of the current  $I_1$  in the term of  $R_i$ ,  $R_1$ ,  $R_2$ ,  $E$  and  $J$ .



### Exercise 2

For the following circuit:

- 1) Find the Thevenin equivalent circuit for the network in the shaded area of the network.
- 2) Find the current through  $R_L$  for values of  $2\ \Omega$ ,  $10\ \Omega$ , and  $100\ \Omega$ .

